


$$V_{I(I)}$$
 $V_{O(S)}$

$$V_0 = I(s) \cdot R$$


$$I = \frac{VI}{1 + R}$$

$$I = \frac{VI}{\frac{1}{SC} + R} \qquad J_0 = \frac{VI}{\frac{1}{SC} + R} \cdot R =$$
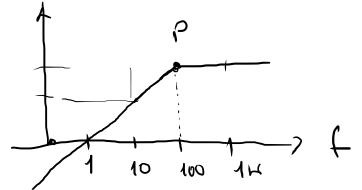
$$F(s) = \frac{Vo}{Vi} = \frac{R}{1 + sRC} = \frac{g \cdot RC}{1 + sRC} \approx \frac{1}{1 + sRC}$$





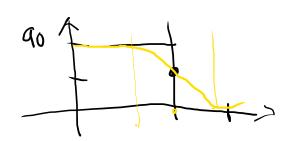

$$\mp(s) = \frac{(s+a)(s+b)}{(s+c)(s+d)(s+e)}$$



