$$\underline{T}_{(S)} = \frac{E}{S} \cdot \frac{1}{(R+SL)} =$$

$$\frac{1}{2}$$
 $\frac{1}{2}$

$$v_{(H)} = L \frac{d_{(H)}}{dt} \rightarrow V_{(S)} = L S I_{(S)}$$

$$\frac{\xi}{S} = IR + I.SL = I(R+SL)$$

$$\frac{1}{s+a} \stackrel{+}{\sim} e$$

$$\frac{I(s)}{s} = \frac{E}{s} \frac{1}{(R+sL)} = \frac{E}{s} \frac{1}{(R+sL)} = \frac{E}{L} \cdot \frac{1}{s(s+R)}$$

$$\frac{1}{s(s+a)} = \frac{1}{a} (1-e^{-at})$$







